

College of Industrial Technology  
King Mongkut's University of Technology North Bangkok



Final Examination of Semester 1

Year: 2012

Subject: 341131 Electrical Drawing I

Section: 5-6

Date: 4 October 2012

Time: 08.00-10.00

Name..... ID..... Field of Study.....

**Instructions**

1. Cheating will result in failure of all classes registered for the current semester.  
Students who are caught cheating will also be denied registering for the following semester.
2. No documents are allowed to be taken out of the examination room.
3. Textbook, calculator and dictionary are NOT allowed.
4. No any electronic communication devices allow in the exam room.
5. The examination has 4 pages (including this page), 1 problem and a total score of 30 points.
6. Write all your answers on this exam sheet.

1. Figure 1 shows a floor plan with one-line diagram, this contained:

- Fluorescent L1 is connected to control S1 and S2 (two-way switches),
- 2 incandescent lamps (E1 and E2) are controlled by switch S3,
- Switch S4 controls fluorescent lamp L2,
- Series switch S5 connects to 2 incandescent lamps (E3 and E4),
- 4 plug sockets,
- kWh meter,
- 16A fuse,
- Load center (LC).

Draw the control diagram of all circuits for this floor plan.

(30 points)

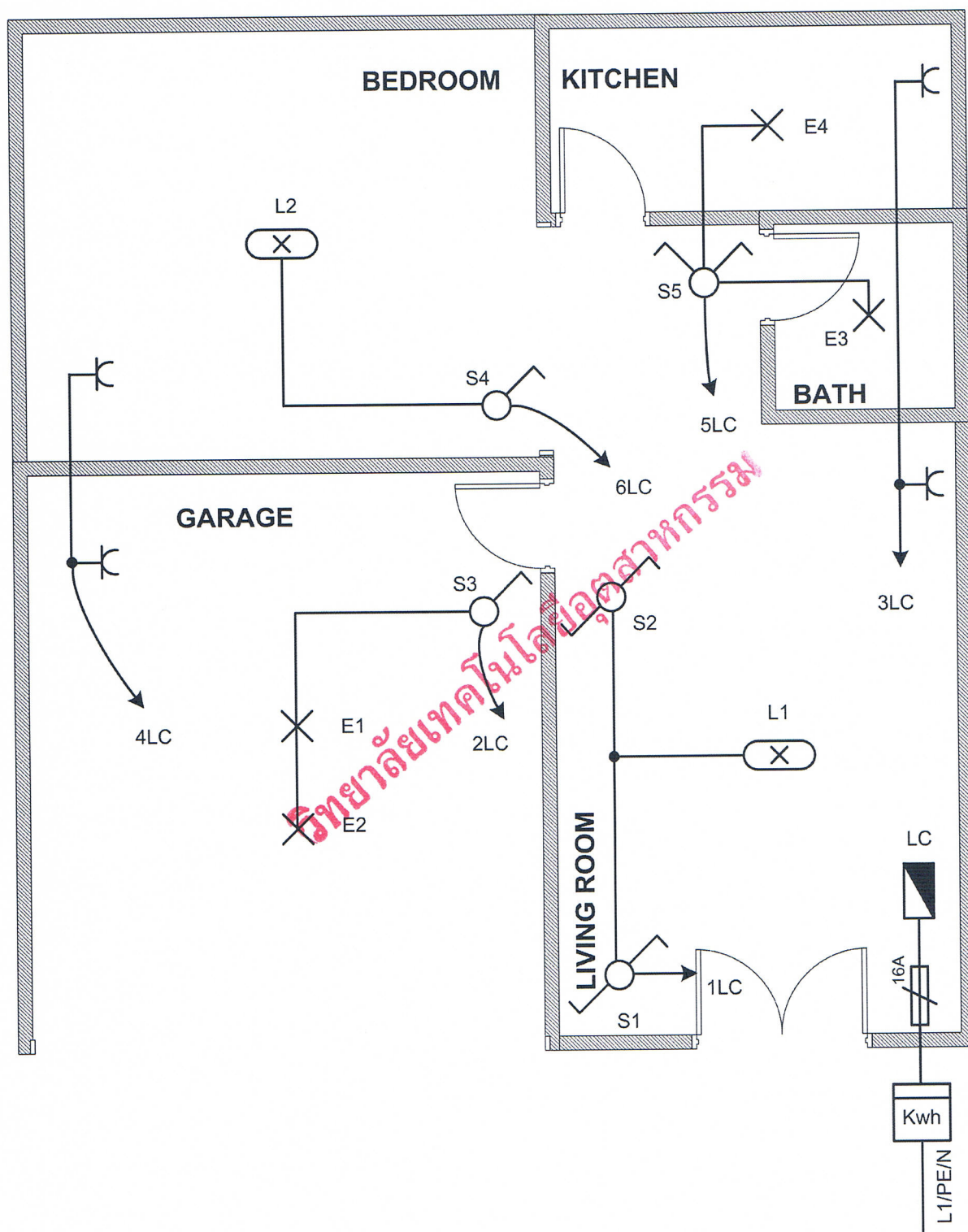


Figure 1

Control diagram

วิทยาลัยเทคโนโลยีอุตสาหกรรม

Control diagram

วิทยาลัยเทคโนโลยีอุตสาหกรรม

Chaichan Kusoljittakorn  
Rattanakorn Phadungthin