

College of Industrial Technology
King Mongkut's University of Technology North Bangkok



Midterm Examination of Semester 1

Year: 2015

Subject: 341131 Electrical Drawing I

Section: 5-6

Date: 12 October 2015

Time: 8.00-10.00

Name..... ID..... EP.....

Instructions


1. Cheating will result in failure of all classes registered for the current semester.
Students who are caught cheating will also be denied registering for the following semester.
2. No documents are allowed to be taken out of the examination room.
3. Textbook, calculator and dictionary are NOT allowed.
4. The examination has 5 pages (including this page), 2 problems and a total score of 50 points.
5. Write all your answers on this exam sheet.

1. Please draw the symbols of the following electrical devices that are used in wiring diagram, one line diagram and control diagram in the table below. (15 points)

Device	Wiring diagram	One line diagram	Control diagram
Switch			
Series Switch			
2-way Switch			

Device	Wiring diagram	One line diagram	Control diagram
Plug Socket			
Incandescent Lamp			

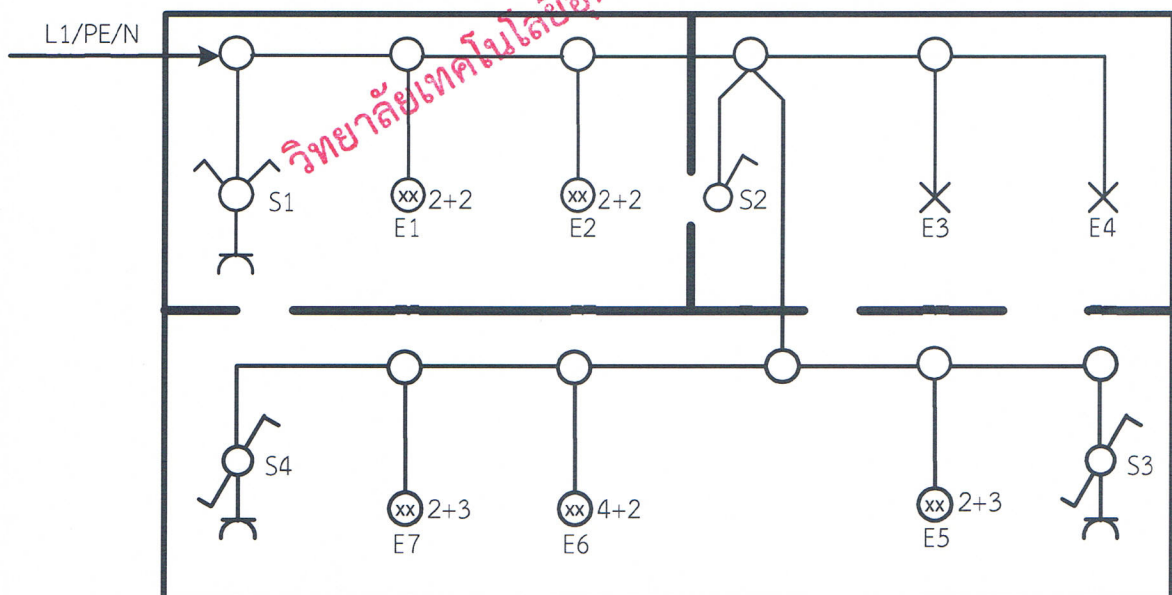2. The floor plan is shown below with electrical circuit diagrams which consist of 5 series incandescent lamps (E1, E2, E5, E6 and E7), 2 incandescent lamps (E3 and E4), 1 series switch (S1), 1 switch (S2), 2 two-way switches (S3, S4) and 3 plug sockets.



Remarks:

- E1 and E2 are controlled by S1.
- E3 and E4 are controlled by S2.
- E5, E6 and E7 are controlled by S3 and S4.
- 3 plug sockets are independent each other.

Please draw the wiring, one-line and control diagrams. (35 points)

341131/3

เลขที่นั่งสอบ

Wiring diagram (15 points) Name.....ID.....

วิทยาลัยเทคโนโลยีอุตสาหกรรม

One-line diagram (10 points) Name.....ID.....

วิทยาลัยเทคโนโลยีอุตสาหกรรม

Control diagram (10 points) Name.....ID.....

วิทยาลัยเทคโนโลยีอุตสาหกรรม