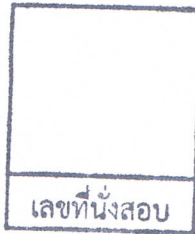


College of Industrial Technology
King Mongkut's University of Technology North Bangkok



Final Examination of Semester 1

Year: 2012

Subject: 353152 Electronic Circuits I

Section: 5-6

Date: 5 October 2012

Time: 10.00-12.00

Name: _____ ID: _____ Field of Study: _____

Instructions:

1. Cheating will result in failure of all classes registered for the current semester. Students who are caught cheating will also be denied registering for the following semester.
2. No documents are allowed to be taken out of the examination room.
3. Text books are NOT allowed.
4. Dictionaries and a calculator are allowed.
5. No any electronic communication devices allow in the exam room.
6. The examination has 11 pages (including this page), 2 parts (55 questions) and a total score of 150 points.
7. Write all your answers on this exam sheet.

วิทยาลัยเทคโนโลยีอุตสาหกรรม

Part 1 (100 points) Multiple choices

Instruction: Mark the correct answer for the following questions in the provided answer sheet.

- Which of following transistor operating mode represents the short circuit?
(A) cut-off (B) saturation (C) active (D) open
- Which class of power amplifiers that conducts less than 180° of input.
(A) class A (B) class B (C) class AB (D) class C
- Which class of power amplifiers having Q-point at the cutoff point.
(A) class A (B) class B (C) class AB (D) class C
- Which class of power amplifiers that conducts through 360° of input.
(A) class A (B) class B (C) class AB (D) class C
- Which of following is true?
(A) EB Junction is forward biased when transistor is in active mode.
(B) EB Junction is forward biased when transistor is in cutoff mode.
(C) CB Junction is reverse biased when transistor is in saturation mode.
(D) CB Junction is forward biased when transistor is in cutoff mode.
- How can the class A amplifier efficiency be improved from 25%?
(A) increase input current. (B) reduce input current.
(C) add transformer at input side. (D) add transformer at output side.
- What is the benefit of using Darlington pair and feedback pair transistors for push-pull operation?
(A) reduce output swing (B) increase output power
(C) increase input current (D) reduce distortion
- Which type of following power amplifiers having the highest efficiency?
(A) class A (B) class B (C) class AB (D) class C

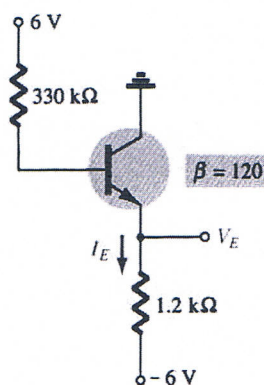


Figure 1.

- From Figure 1, find the current I_B .
(A) $23.78 \mu\text{A}$ (B) 23.78 mA (C) $34.11 \mu\text{A}$ (D) 34.11 mA
- From Figure 1, find the current I_E .
(A) $2.87 \mu\text{A}$ (B) 2.87 mA (C) $4.12 \mu\text{A}$ (D) 4.12 mA

Figure 2.

11. From Figure 2, find the current I_B .
- (A) $80.16 \mu A$ (B) $80.16 mA$ (C) $45.73 \mu A$ (D) $45.73 mA$
12. From Figure 2, which of following equations is for finding V_{CE} ?
- (A) $V_{CE} = V_{EE} - 0.7 - I_E R_E$ (B) $V_{CE} = V_{EE} - I_E R_E$
(C) $V_{CE} = V_{EE} - I_E R_E - I_B R_B$ (D) $V_{CE} = V_{EE} - I_E R_E - 0.7 - I_B R_B$

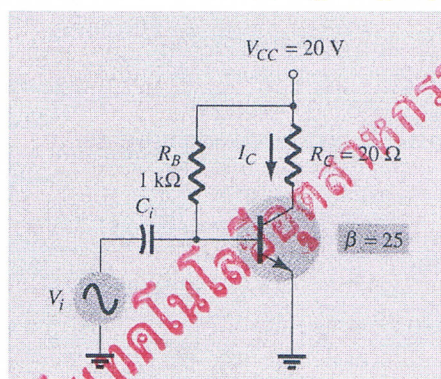


Figure 3.

13. From Figure 3, what is value of $P_o(AC)$ if $I_c = 250$ mA peak?
(A) 1.25 mW (B) 1.25 W (C) 0.625 mW (D) 0.625 W
14. What is the cause of crossover distortion in push-pull circuit?
(A) two transistors do not turn on/off simultaneously.
(B) heat at transistor.
(C) two transistors are not the same type (PNP and NPN).
(D) input current is the sine wave.
15. What is the value of I_{DC} of class B amplifier if peak output current $I_L(p)$ is 1 A.
(A) 0.318 A (B) 0.636 A (C) 0.707 A (D) 1.414 A
16. What is the value of $P_o(AC)$ of class B amplifier if $V_L(p-p) = 10$ V and $R_L = 2$ ohms.
(A) 50 W (B) 25 W (C) 6.25 W (D) 5.25 W
17. What is the purpose of using push-pull circuit for class B amplifier?
(A) to obtain full cycle (B) to reduce the distortion
(C) to increase speed of signal (D) to reduce the cost of amplifier
18. For the most dc configurations, following law is used.
(A) KCL (B) KVL (C) Ohm (D) Lenz

19. What is the equation when the transistor is operating in saturation mode?

(A) $I_C = \frac{V_{CC}}{R_C}$

(B) $V_{CE} = V_{CC}$

(C) $I_B = \frac{V_{CC} - V_{BE}}{R_B}$

(D) $V_{CE} = V_{EE} - I_E R_E$

20. What is the equation when the transistor is operating in cut-off mode?

(A) $I_C = \frac{V_{CC}}{R_C}$

(B) $V_{CE} = V_{CC}$

(C) $I_B = \frac{V_{CC} - V_{BE}}{R_B}$

(D) $V_{CE} = V_{EE} - I_E R_E$

21. What is efficiency of class A amplifier?

(A) $\% \eta = \frac{P_o(dc)}{P_i(dc)} \times 100\%$

(B) $\% \eta = \frac{P_o(ac)}{P_i(dc)} \times 100\%$

(C) $\% \eta = \frac{P_o(dc)}{P_i(ac)} \times 100\%$

(D) $\% \eta = \frac{P_o(ac)}{P_i(ac)} \times 100\%$

22. For the most dc configuration, the analysis will start by _____.

(A) base current

(B) emitter current

(C) collector current

(D) emitter-collector voltage

23. Which of following circuits, emitter is connected directly to the ground.

(A) fixed-bias

(B) emitter-bias

(C) emitter-follower

(D) collector feedback

24. Which of the following is NOT the application of a transistor?

(A) Amplification of signal

(B) Switching and control

(C) Computer logic circuitry

(D) Fluorescents

25. In an emitter-bias configuration, the _____ the resistance R_E , the _____ the stability factor, and the _____ stable is the system.

(A) smaller, lower, less

(B) larger, more, more

(C) smaller, more, more

(D) larger, lower, more

26. In a transistor-switching network, the level of the resistance between the collector and emitter is _____ at the saturation and is _____ at the cutoff.

(A) low, low

(B) low, high

(C) high, high

(D) high, low

27. Calculate the delay time in a transistor switching network if t_{on} is 56 ns, t_r = 14 ns, and t_f = 20 ns.

(A) 70 ns

(B) 42 ns

(C) 36 ns

(D) 34 ns

28. The ____ the stability factor, the ____ sensitive the network is to variations in that parameter.
- (A) higher, more (B) higher, less
(C) lower, more (D) None of the above
29. In a transistor-switching network, the operating point switches from ____ to ____ regions along the load line.
- (A) cutoff, active (B) cutoff, saturation
(C) active, saturation (D) None of the above
30. ____ is the primary difference between the exact and approximate techniques used in the analysis of a voltage divider circuit.
- (A) Thevenin voltage E_{Th} (B) Thevenin resistance R_{Th}
(C) Base voltage V_B (D) R_C
31. ____ is the least stabilized circuit.
- (A) Fixed bias (B) Emitter-stabilized bias
(C) Voltage divider (D) Voltage feedback
32. ____ is less dependent on the transistor beta.
- (A) Fixed bias (B) Emitter-stabilized bias
(C) Voltage divider (D) Voltage feedback
33. The Thevenin equivalent network is used in the analysis of the ____ circuit.
- (A) Fixed bias (B) Emitter-stabilized bias
(C) Voltage divider (D) Voltage feedback
34. The emitter resistor in an emitter-stabilized bias circuit appears to be ____ in the base circuit.
- (A) larger (B) smaller
(C) the same (D) none of the above
35. Changes in temperature will affect the level of ____.
- (A) current gain β (B) leakage current I_{CEO}
(C) both current gain β and leakage current I_{CEO} (D) None of the above
36. In any amplifier employing a transistor, the collector current I_C is sensitive to ____.
- (A) β (B) V_{BE} (C) I_{CO} (D) All of the above
37. Class D operation can achieve power efficiency of over ____.
- (A) 90% (B) 78.5% (C) 50% (D) 25%

38. In order to isolate the ac levels from the dc analysis in a transistor network, the capacitor can be replaced by _____.

- (A) an open circuit equivalent (B) a short circuit equivalent
(C) a voltage source (D) a current source

39. Calculate V_{CEQ} from Figure 4.

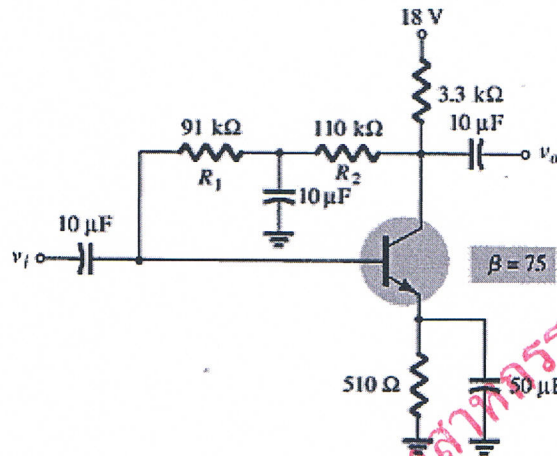


Figure 4.

- (A) 8.78 V (B) 0 V (C) 7.86 V (D) 18 V

40. As the temperature increases, β _____, V_{BE} _____, and I_{CO} _____ in value for every 10°C .

- (A) increases, decreases, doubles
(B) decreases, increases, remains the same
(C) decreases, increases, doubles
(D) increases, increases, triples

41. Which type of amplifier uses pulse (digital) signals in its operation?

- (A) Class A (B) Class B or AB
(C) Class C (D) Class D

42. In a voltage-divider circuit, which one of the stability factors has the least effect on the device at very high temperature?

- (A) $S(I_{CO})$ (B) $S(V_{BE})$ (C) $S(\beta)$ (D) Undefined

43. In a fixed-bias circuit, which one of the stability factors overrides the other factors?

- (A) $S(I_{CO})$ (B) $S(V_{BE})$ (C) $S(\beta)$ (D) Undefined

44. Which of the following voltages must have a negative level (value) in any NPN bias circuit?

- (A) V_{BE} (B) V_{CE} (C) V_{BC} (D) None of the above

45. For the typical transistor amplifier in the active region, V_{CE} is usually about ____ % to ____ % of V_{CC} .
- (A) 0, 100 (B) 25, 75 (C) 45, 55 (D) 50, 50
46. In a collector feedback bias circuit, the current through the collector resistor is ____ and the collector current is ____.
- (A) I_C , I_C (B) $I_B + I_C$, I_C
 (C) I_B , I_C (D) None of the above
47. For a transistor operating in the saturation region, the collector current I_C is at its ____ and the collector-emitter voltage V_{CE} is to the ____.
- (A) minimum, left of the V_{CEsat} line (B) minimum, right of the V_{CEsat} line
 (C) maximum, left of the V_{CEsat} line (D) maximum, right of the V_{CEsat} line
48. How many transistors must be used in a class B power amplifier to obtain the output for the full cycle of the signal?
- (A) 0 (B) 1 (C) 2 (D) 3
49. A heat sink provides ____ thermal resistance between case and air.
- (A) a high (B) a low
 (C) the same (D) None of the above
50. A ____ power amplifier is limited to use at one fixed frequency.
- (A) class A (B) class B or AB
 (C) class C (D) class D

Part 2 (25 points) Calculation

Instruction: Show the mathematical expression and answers of following problems.

1. From Figure 5, calculate the input power $P_i(\text{dc})$ and output power $P_o(\text{ac})$ of the circuit. The input signal results in a base current of $5 \text{ mA}_{\text{RMS}}$, where $\beta = 50$ and $V_{CC} = 20 \text{ V}$

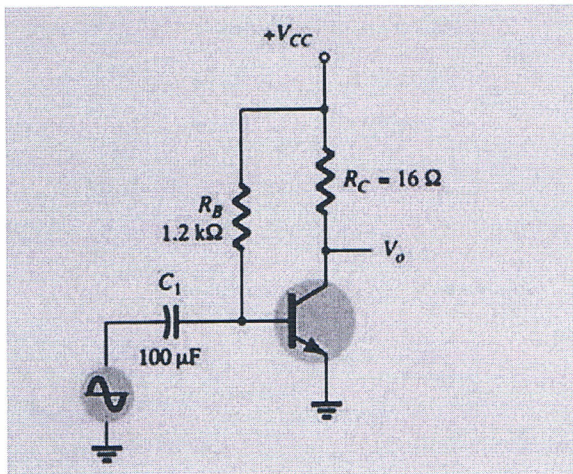


Figure 5.

2. From Figure 6, determine the level of V_{CE} and I_B and for the network with $\beta = 100$.

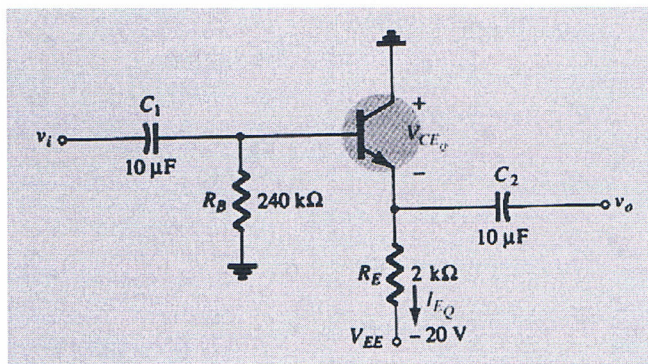


Figure 6.

3. From Figure 7, determine I_B , V_B , and V_E with $\beta = 100$

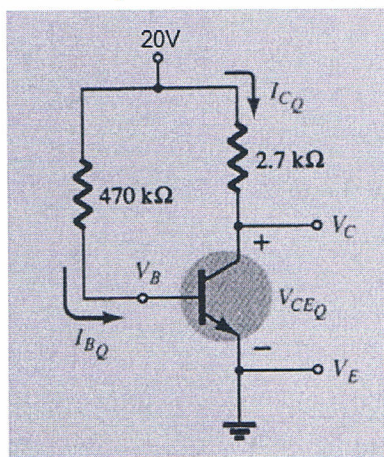


Figure 7.

4. Use this table below to determine the change in I_C from 25°C to 100°C for $R_B / R_E = 70$ due to the $S(I_{CO})$

stability factor. Assume an emitter-bias configuration where $S(I_{CO}) = \frac{(\beta+1)\left(1+\frac{R_B}{R_E}\right)}{(\beta+1)+\frac{R_B}{R_E}}$.

T (°C)	I_{CO} (nA)	β	V_{BE} (V)
-65	0.2×10^{-3}	20	0.85
25	0.1	50	0.65
100	20	80	0.48
175	3.3×10^3	120	0.3

5. Calculate R_{th} , E_{th} and V_B from Figure 8.


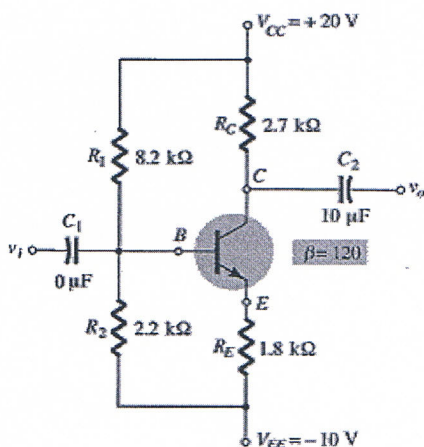


Figure 8.

Handout


Emitter-follower

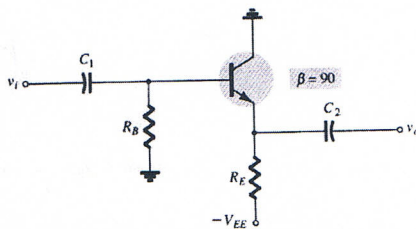

$$V_{CE} = V_{EE} - I_E R_E$$

$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1)R_E}$$


Collector-feedback

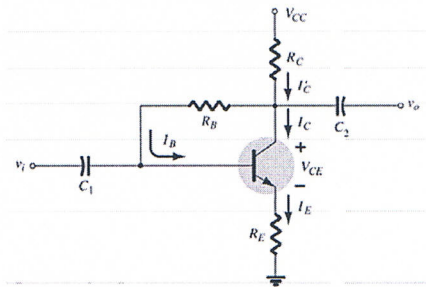

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

Common-base

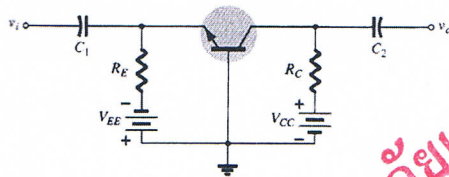

$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$V_{CE} = V_{EE} + V_{CC} - I_E(R_C + R_E)$$

Class A amplifier

$$P_i(DC) = \frac{V_{CC}^2}{2R_C}$$

$$P_o(AC) = \frac{V_{CC}^2}{8R_C}$$

Transformer-couple class A amplifier

$$\%h = 50 \left(\frac{V_{CE(max)} - V_{CE(min)}}{V_{CE(max)} + V_{CE(min)}} \right)^2$$

$$\frac{R'_L}{R_L} = \frac{R_1}{R_2} = \left(\frac{N_1}{N_2} \right)^2 = a^2$$

Class B amplifier

$$P_o(AC) = \frac{V_L^2(p-p)}{8R_L} = \frac{V_L^2(p)}{2R_L}$$

$$P_i(DC) = V_{CC} I_{dc} = V_{CC} \left(\frac{2}{\pi} I_L(p) \right)$$

Answer Sheet

เลขที่นั่งสอบ

Name: _____ ID: _____

Subject: 342152 Electronic Circuits I

	(A)	(B)	(C)	(D)
1.				
2.				
3.				
4.				
5.				
6.				
7.				
8.				
9.				
10.				
11.				
12.				
13.				
14.				
15.				
16.				
17.				
18.				
19.				
20.				
21.				
22.				
23.				
24.				
25.				

	(A)	(B)	(C)	(D)
26.				
27.				
28.				
29.				
30.				
31.				
32.				
33.				
34.				
35.				
36.				
37.				
38.				
39.				
40.				
41.				
42.				
43.				
44.				
45.				
46.				
47.				
48.				
49.				
50.				